

Registers:-

Parallel Register is a Flip Flop, but it takes input of n-bit.

※ VHDL Code of Register with Asynchronous rst.

entity reg is

Port(din : in std_logic_vector(3 downto 0);

clk, rst : in std_logic;

dout : out std_logic_vector(3 downto 0);

end entity reg;

architecture rtl of reg is

begin

process(rst, clk)

begin

if (rst = '1') then

dout <= (others => '0'); // Initial state


elsif (rising_edge(clk)) then

dout <= din;

endif;

end process;

end rtl;

 

Shift Registers:-

① Shift right register.

② Shift left register.

Shift register performs two operations:-

① Load data


② Shift data

left
right

We use control signal, "load", to choose which operation will be performed.

if load \leq '1' \rightarrow load data.

if load \leq '0' \rightarrow shift data.

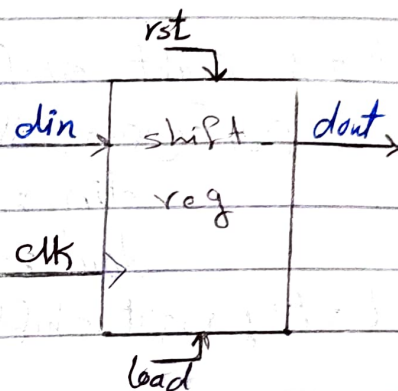

* shift right with n bits \approx divide by 2^n

* shift left with n bits \approx multiply by 2^n

mode: in \approx internal signal		mode: out \approx internal signal
------------------------------------	--	-------------------------------------

in assign operator "=":


Signal which is defined as input, ~~can't~~ should be written in Left, and it can't be in Right. and the opposite for output signal. $dout \leftarrow \underline{dout} (2 \text{ downto } 0);$

So, we will use temp internal signal to be able to use value of output signal in the right.

We can't use buffer mode because connected other circuits.

OIP ~~mode~~ signal type = input port type. "mode".

Shift Right Register:-

 

VHDL Code with Asynchronous rst:

entity right_shift_reg is

port (rst, clk, load: in std_logic;

 din: in std_logic_vector (3 downto 0); load

 dout: out std_logic_vector (3 downto 0));

end entity right_shift_reg;

architecture rtl of right_shift_reg is

 signal d_temp: std_logic_vector (3 downto 0);

begin

 process (rst, clk)

 begin

 if (rst = '1') then

 d_temp <= (others => '0');

 elsif (rising_edge (clk)) then

 if (load = '1') then

 * Read data operation.

 d_temp <= din;

 else

 * Shift data operation.

 d_temp <= '0' & d_temp (3 downto 1);

 endif;


 end if;

end process;

 dout <= d_temp;

end architecture rtl;

Shift Left Register:-

 

VHDL - Code with Asynchronous rst:- "shift left 3bits"

entity left_shift_reg is

Port (rst, clk, load: in std_logic;

din: in std_logic_vector(7 downto 0);

dout: out std_logic_vector(7 downto 0));

end entity left_shift_reg;

architecture rtl of left_shift_reg is

Signal d_temp: std_logic_vector(7 downto 0);

begin

process (rst, clk)

^{begin} if (rst = '1') then

d_temp <= (others => '0');

elsif (rising_edge(clk)) then

if (load = '1') then

d_temp <= din;

else

d_temp <= d_temp(4 downto 0) & "000";

end if;

end if;

end process;

dout <= d_temp;

end architecture rtl;

Shift left & right register:-

VHDL Code with Asynchronous rst:-

load "00"	load data
"01"	shift data to right
"10"	shift data to left

entity shift_reg is

```

Port (rst, clk, load: in std_logic;
      load      : in std_logic_vector (1 downto 0);
      din       : in std_logic_vector (3 downto 0);
      dout      : out std_logic_vector (3 downto 0));

```

end entity shift_reg;

architecture rtl of shift_reg is

Signal d_temp: std_logic_vector (3 downto 0);

begin

process (rst, clk)

if (rst = '1') then

d_temp <= ~~others~~ (others => '0');

elsif (rising_edge (clk)) then

if (load = "00") then * load data

d_temp <= din;

elsif (load = "01") then * shift data to right

d_temp <= '0' & d_temp (3 downto 1);

elsif (load = "10") then * shift data to left

d_temp <= d_temp (2 downto 0) & '0';

endif;

endif;

end process;

dout <= d_temp;

end architecture rtl;